Thomas Puskas
Circuits 2 lab 02
KUID: 2026962128

Experiment 2: Differential amplifiers

Objective: To understand the uses and physics behind differential amplifiers which are designed to amplify the difference between two signals. We seek to understand differential mode gain vs common mode to differential conversion. Lastly, we also will study feedback and use it in the experiment.

Materials: 1kOhm resistor x3, 1.2kOhm resistor x1, NMOS 2N7000 x 4, CS-147 transformer x 1

3.1 Differential signals

$$Vov = Vgs - Vth = (5 - 3.2675) - 1.6 = 0.1325V$$

$$gm1 = \frac{2ID}{Vov} = \frac{2\ x\ 8.12\ x\ 10^{-3}}{0.1325} = 122.57\ x\ 10^{-3}\ A/V$$

$$gm2 = \frac{2ID}{Vov} = \frac{2\ x\ 6.47\ x\ 10^{-3}}{0.1325} = 97.66\ x\ 10^{-3}\ A/V$$

$$gm = \frac{gm1 + gm2}{2} = 110.12\ x\ 10^{-3}\ A/V$$

Rout [kΩ]	Ad [V/V]
1	110.12

A_d - gmR_{out} = $110.12\ x\ 10^{-3}\ A/V$ x 1000 = 110.12 V

Voltage at which the distortion exists: 0-2V and 13-14V

3.3

V_{out+} [V_{pp}]	V_{out-}[V_{pp}]	V_{out}[V_{pp}]	A_d [V/V]
1.24	1.44	2.68	12.88

V_{CM} [V]	V_{out}[V]	A_{CM-DM} [V/V]
5V	0.138	0.06
5.1	0.144	

$$ACM - DM = \frac{\Delta Vout}{\Delta VCM} = \frac{0.144-0.138}{5.1-5} = \frac{0.006}{0.1} = 0.06\,V/V$$

CMRR [dB]
46.64


$$20log_{10}\left|\frac{Ad}{ACM-DM}\right| = 20log_{10}\left|\frac{12.88}{0.06}\right| = 46.64$$

3.1

V_{in}0 [Vpp]
0.208

V_{CM} + ½ V_{in} [V_{pp}]	V_{CM}- ½ V_{in} [V_{pp}]
0.092	0.094

V_{in} [Vpp]	V_{out+} [V_{pp}]	V_{out-}[V_{pp}]	V_{out}[V_{pp}]	A_d [V/V]
0.208	3.50	4.16	7.66	36.83

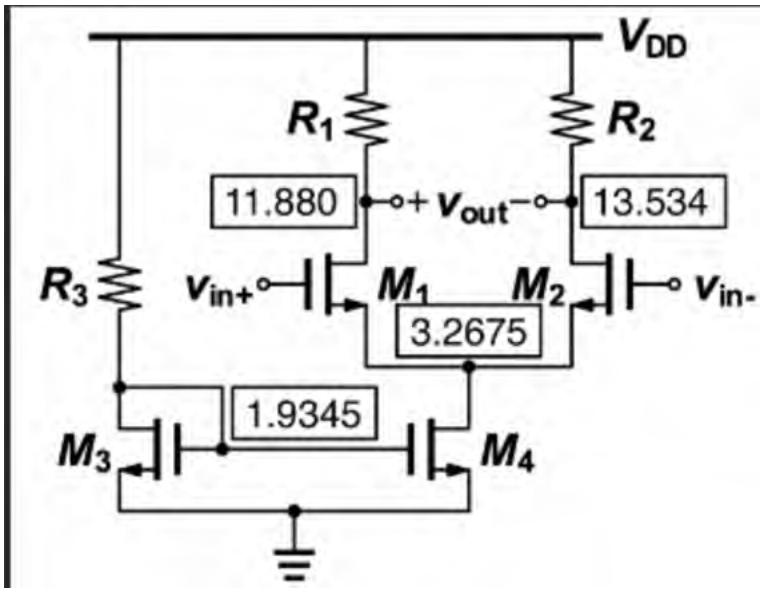


I_{D1} [mA]	I_{D2} [mA]
8.12	6.47


$$Id1 = \frac{VDD - 11.880}{R1} = 8.12\,mA$$

$$Id2 = \frac{VDD - 13.534}{R2} = 6.47\,mA$$

G_{m1} [mA/V]	G_{m2} [mA/V]	G_m [mA/V]
112.57	97.66	110.12


Photos:

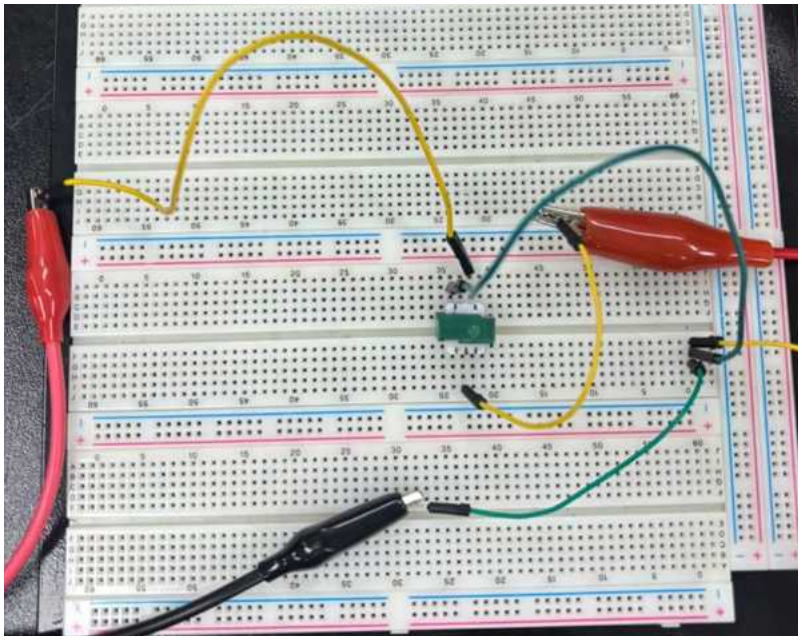

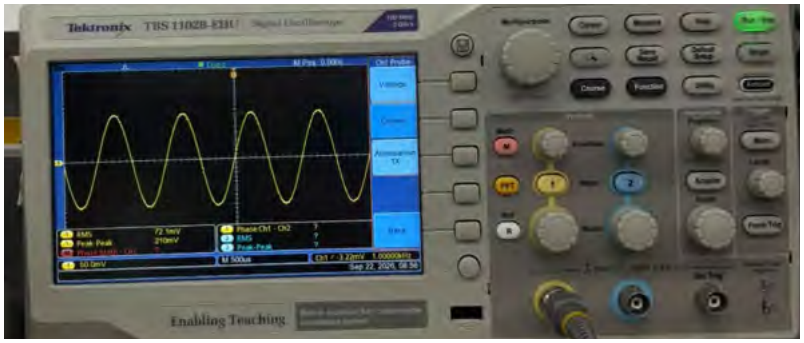

Tektronix
TBS 1102B-EDU
Enabling Teaching

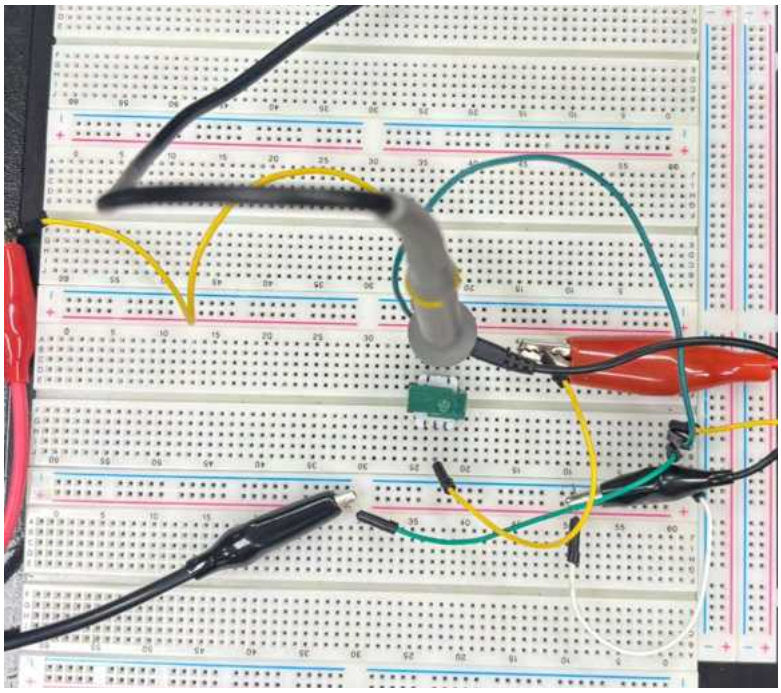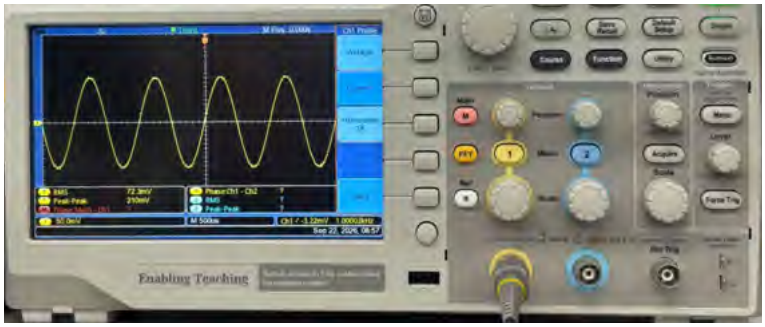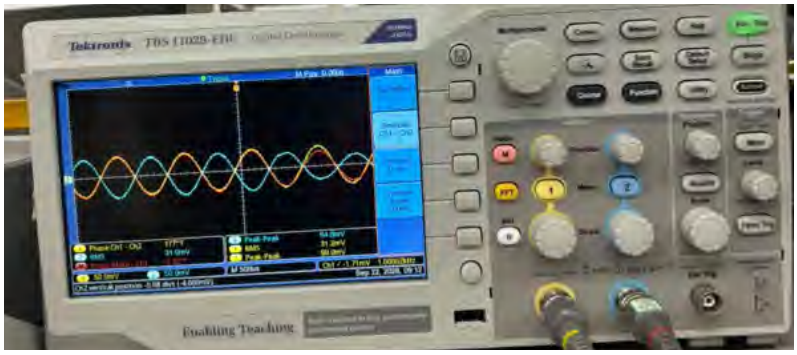

KEITHLEY
2231A-30-3 TRIPLE CHANNEL DC POWER SUPPLY
SELECT
CH1
CH2
CH3
V-Set
I-Set
POWER
OUTPUT
Menu
On/Off
LOCAL
Esc
Enter
Save
Recall








Next Experiment:




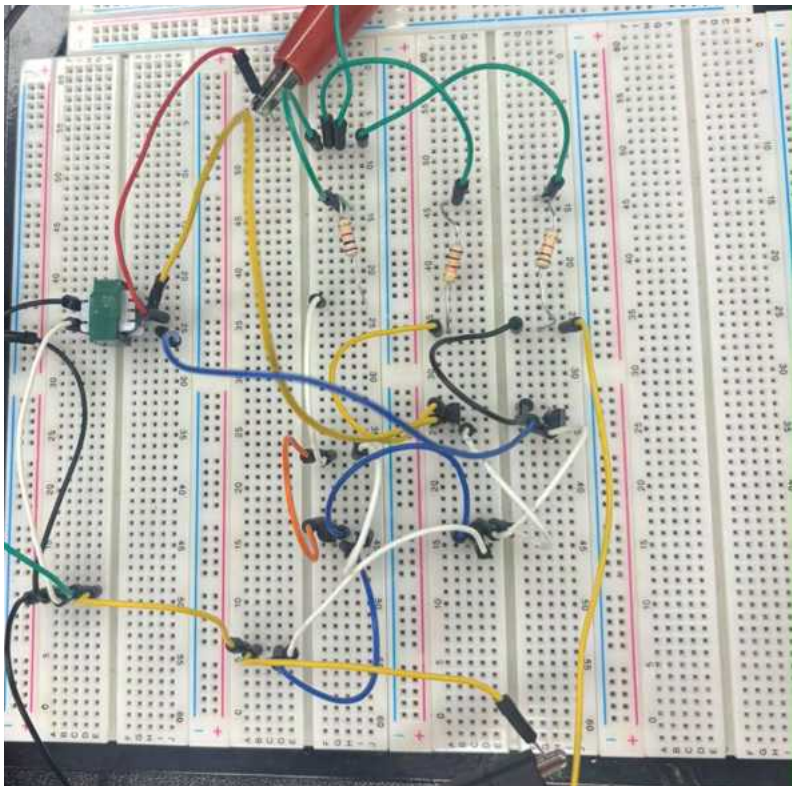

Tektronix
TBS 1102B-EDU
Enabling Teaching



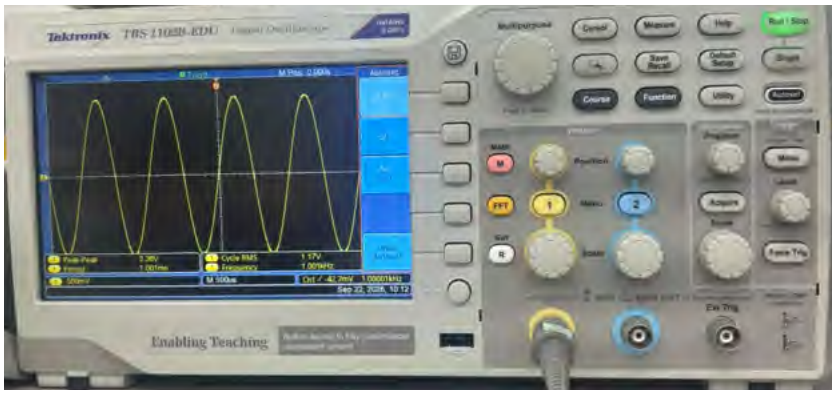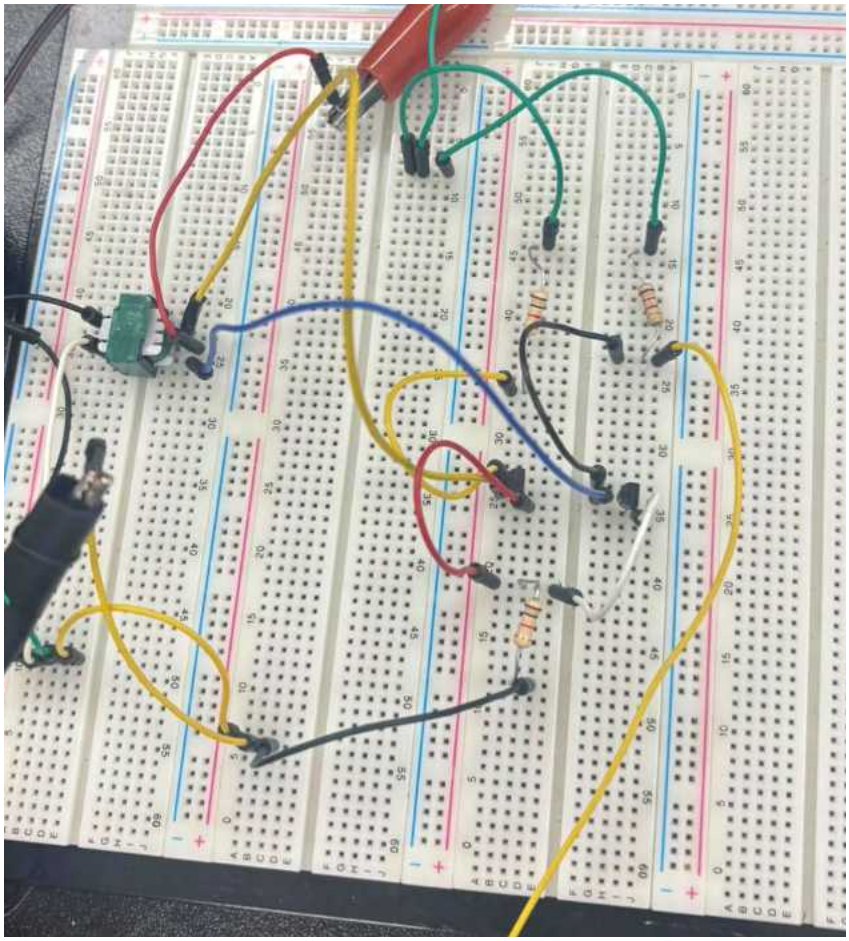

Tektronix
TBS 1102B-EDU
Enabling Teaching




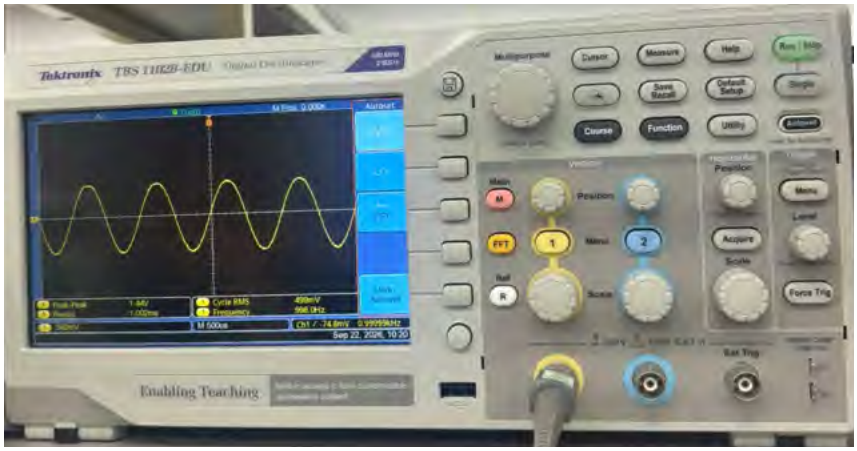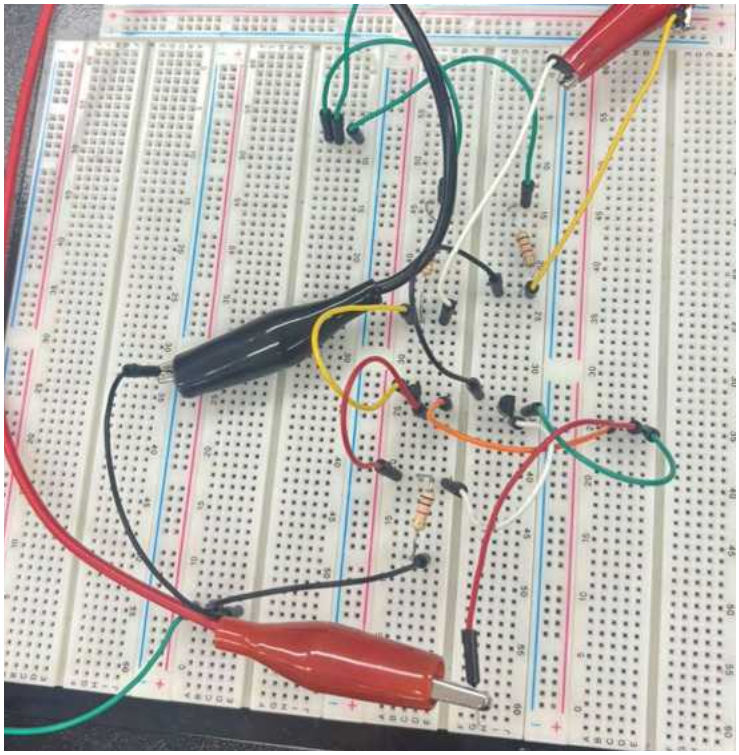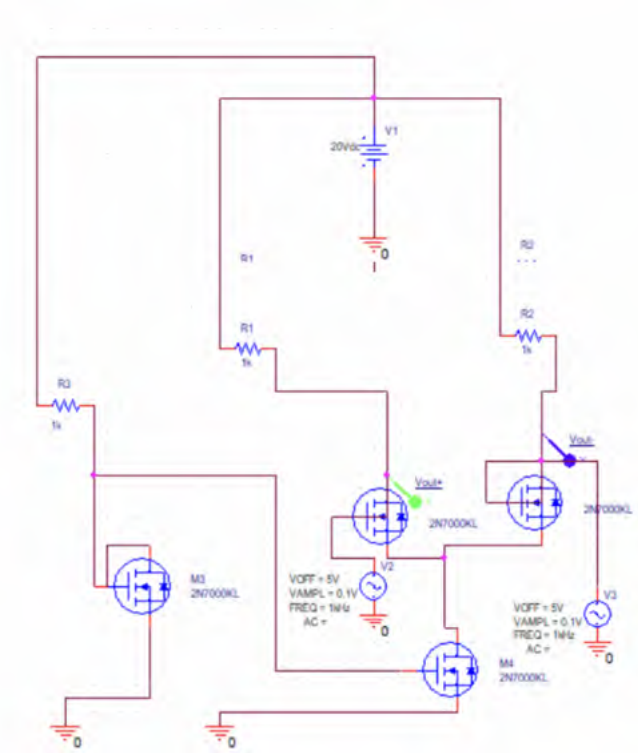
Tektronix
TBS 1102B-EDU
Enabling Teaching



PSPICE


V1
20Vdc
0
R1
R1
1k
R2
R2
1k
R3
1k
Vout-
Vout+
2N7000KL
2N7000KL
M3
2N7000KL
V2
VOFF = 5V
VAMPL = 0.1V
FREQ = 1kHz
AC =
0
V3
VOFF = 5V
VAMPL = 0.1V
FREQ = 1kHz
AC =
0
M4
2N7000KL
0
0

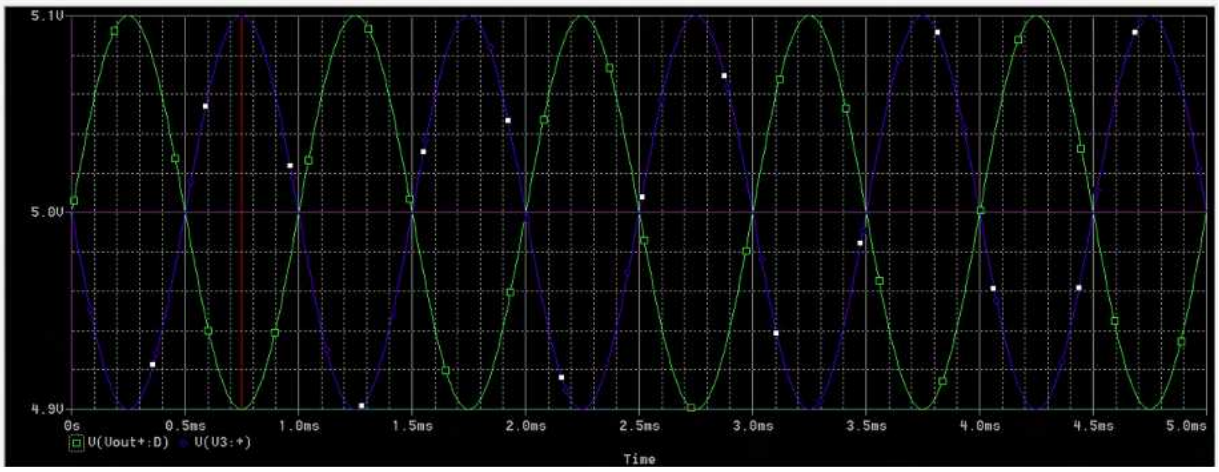
5.1V
5.0V
4.9V
0s
0.5ms
1.0ms
1.5ms
2.0ms
2.5ms
3.0ms
3.5ms
4.0ms
4.5ms
5.0ms
V(Vout+:D)
V(V3:+)
Time